



DEBOUNCER



Mini project





Eng Omar Mahmoud Elsayed Gabr

Passed 4 test cases :


case 1: testing noise then high input

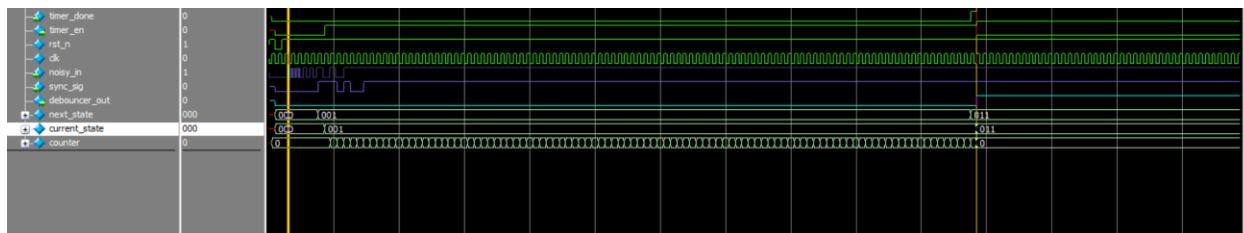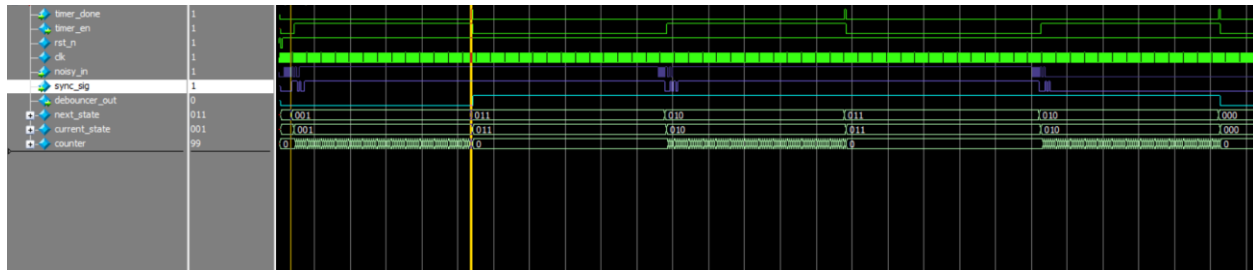

case 2 : testing glitch input while being in high state

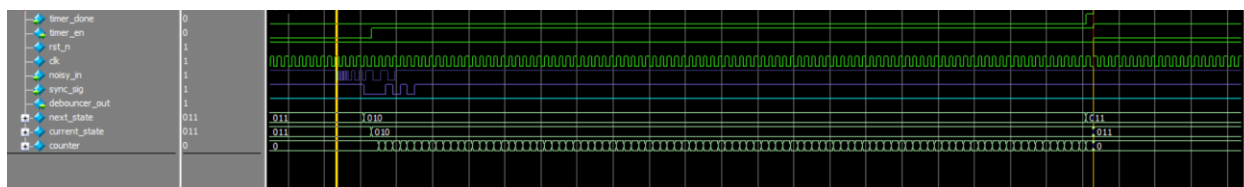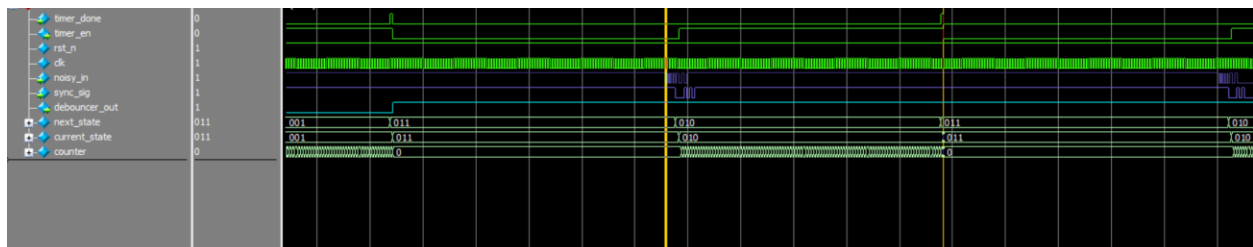

case 3: testing noise then low input

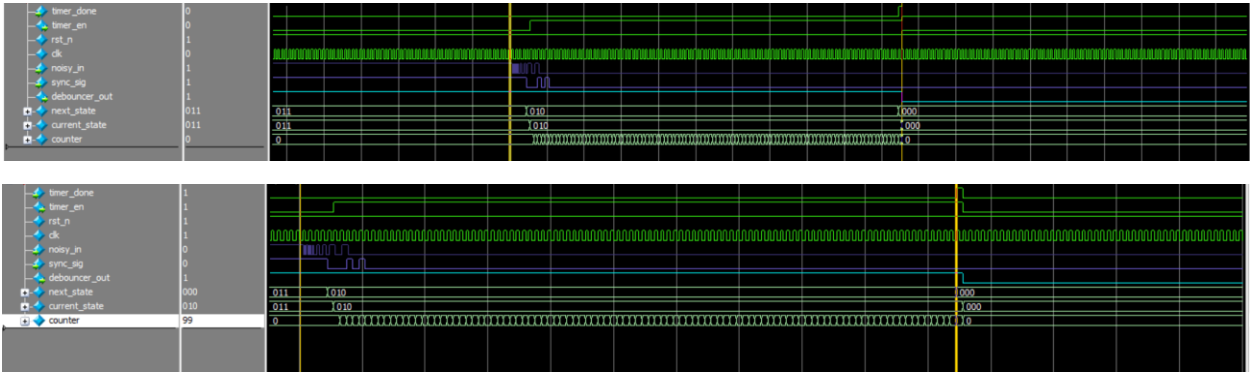

case 4 : testing glitch input while being in low state

